

Single-supply, high-input voltage, full-wave rectifier circuit




Amplifiers

Design Goals

Input	Output	Frequency	Supply	
V_{iMax}	V_{oMax}	f_{Max}	V_{cc}	V_{ee}
9Vpp	4.5Vpp	50kHz	5V	0V

Design Description

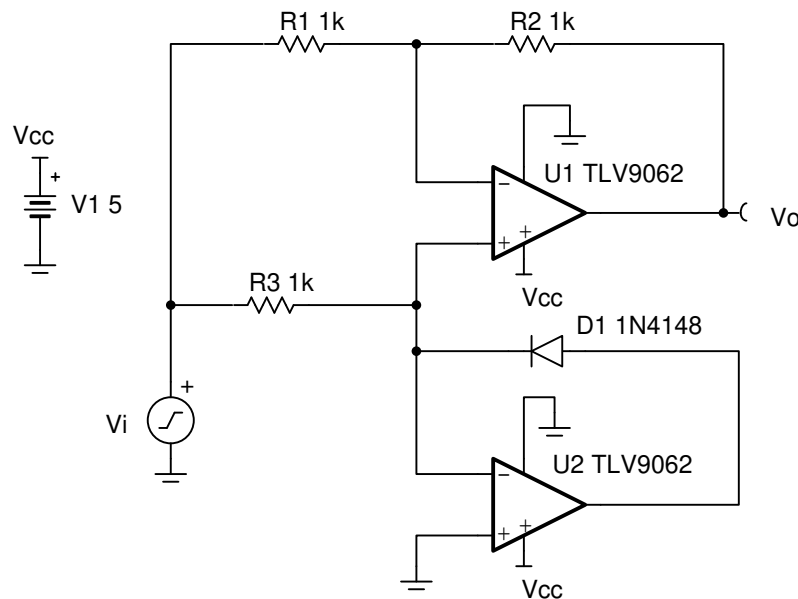This single-supply precision full-wave rectifier is optimized for high-input voltages. When $V_i > 0V$, D_1 is reverse biased and the top part of the circuit, U1, is activated resulting in a circuit with a gain of $1V/V$. When $V_i < 0V$, D_1 is forward biased and the bottom part of the circuit, U2, is activated resulting in an inverting amplifier circuit with a gain of $-1V/V$.




Design Notes

1. Observe common-mode and output swing limitations of op amps.
2. R_3 should be sized small enough that the leakage current from D_1 does not cause errors for positive input cycles while ensuring the op amp can drive the load.
3. Use a fast switching diode for D_1 .
4. Resistor tolerance determines the gain error of the circuit.
5. Use a negative charge pump (such as the [LM7705](#)) for output swing requirements to GND to maintain linearity for output signals near 0V. For additional information, see [Single-supply, low-input voltage, full-wave rectifier circuit](#).
6. For more information on op amp linear operating region, stability, capacitive load drive, driving ADCs, and bandwidth please see the [Design References](#) section.

Design Steps

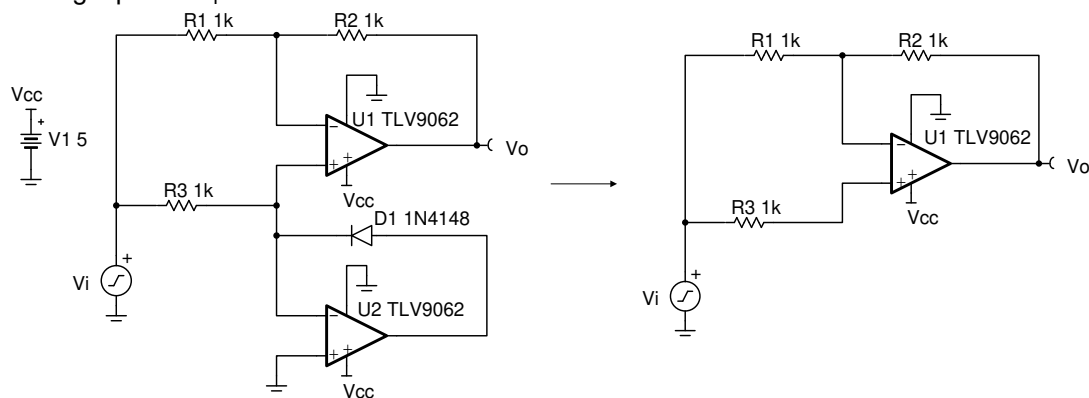
1. Circuit analysis for positive input signals. D_1 is reverse-biased disconnecting the output of U_2 from the non-inverting input of U_1 .



$$\frac{V_o}{V_i} = \left(-\frac{R_2}{R_1} \right) + \left(1 + \frac{R_2}{R_1} \right) = 1$$

$$V_o = V_i$$

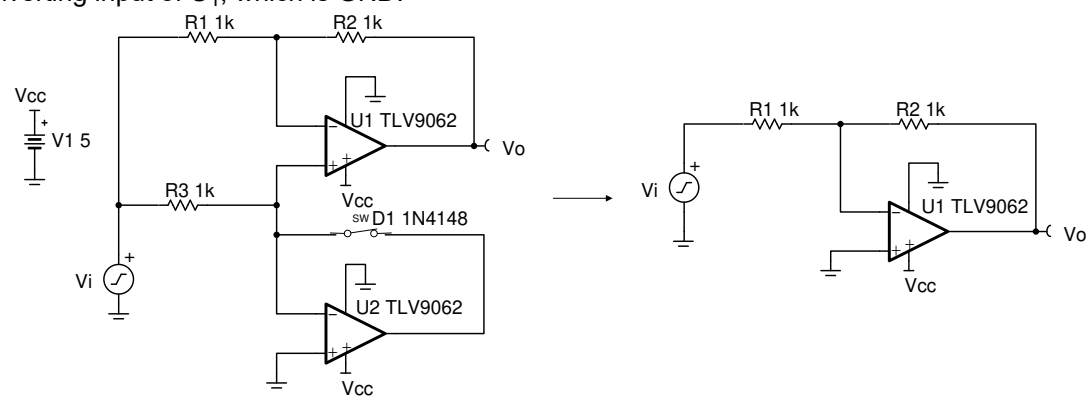2. Circuit analysis for negative input signals. D_1 is forward biased, which connects the output of U_2 to the non-inverting input of U_1 , which is GND.



$$\frac{V_o}{V_i} = \left(-\frac{R_2}{R_1} \right) = -1$$

$$V_o = -V_i$$

3. Select R_1 , R_2 , and R_3 .

$$\frac{V_o}{V_i} = -\frac{R_2}{R_1}$$


$$\text{If } R_2 = R_1 \text{ then } V_o = -V_i$$

$$\text{Set } R_1 = R_2 = R_3 = 1\text{k}\Omega$$


Design Simulations

Transient Simulation Results

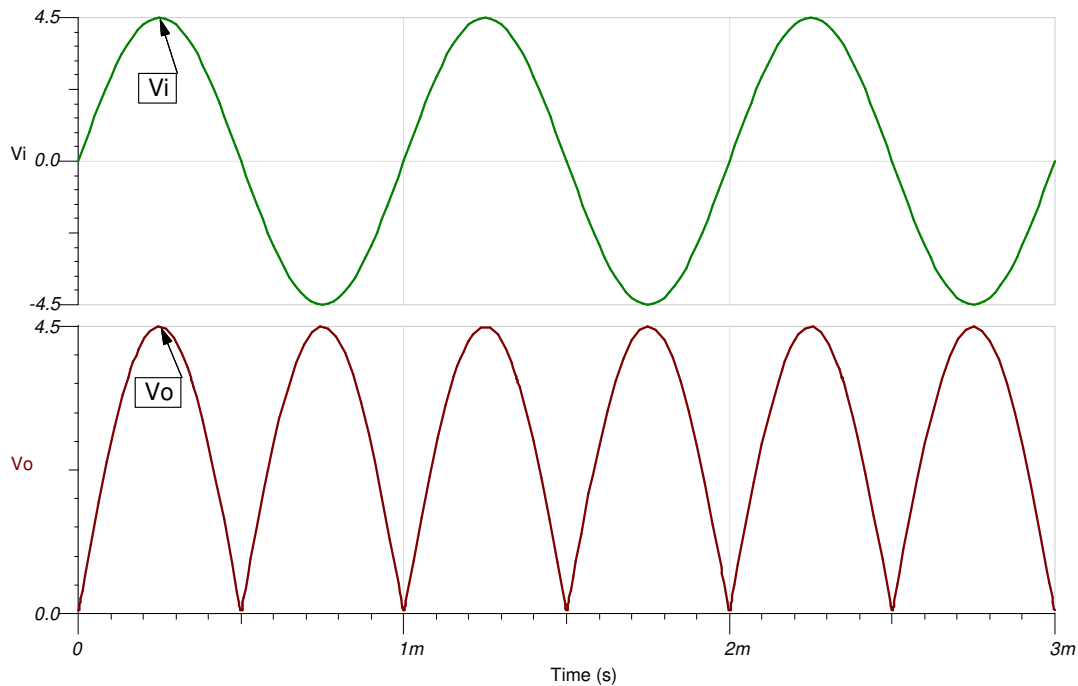A 1-kHz, 9-V_{pp} sine wave yields a 4.5-V_{pp} output sine wave.



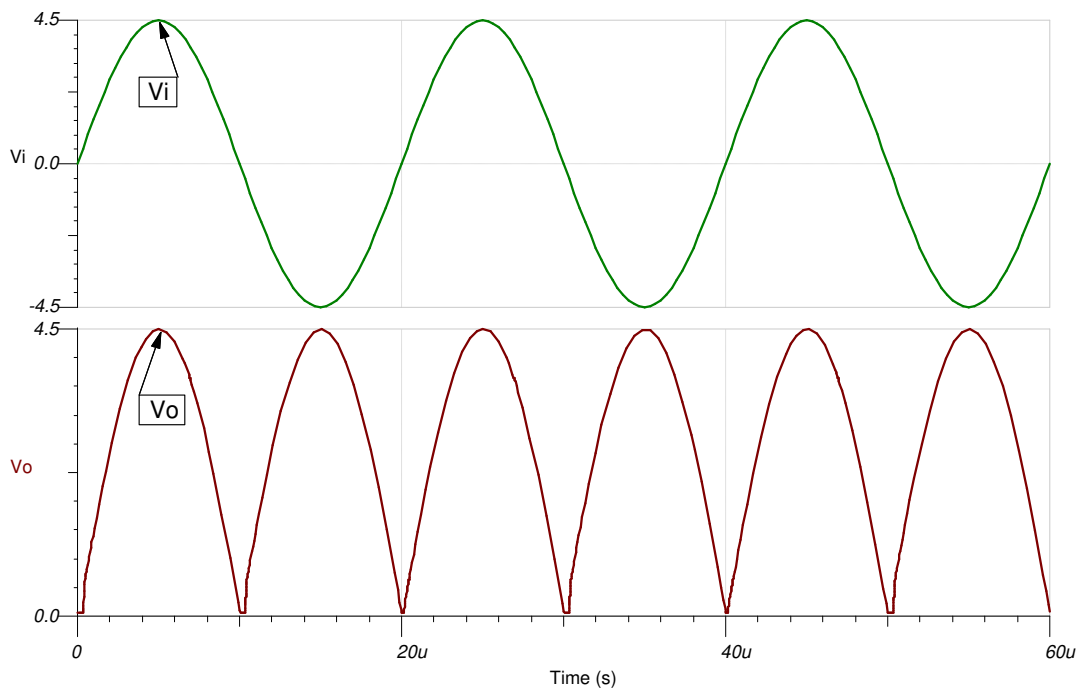A 50-kHz, 9-V_{pp} sine wave yields a 4.5-V_{pp} output sine wave.



Design References

1. See [Analog Engineer's Circuit Cookbooks](#) for the comprehensive TI circuit library.
2. SPICE Simulation File [SBOC529](#).
3. [TI Precision Labs](#)
4. See the [Single-Supply Low-Input Voltage Optimized Precision Full-Wave Rectifier Reference Design](#).

Design Featured Op Amp

TLV9062	
V_{SS}	1.8V to 5.5V
V_{inCM}	Rail-to-rail
V_{out}	Rail-to-rail
V_{os}	0.30mV
I_q	538 μ A
I_b	0.5pA
UGBW	10MHz
SR	6.5V/ μ s
#Channels	1, 2, 4
www.ti.com/product/TLV9062	

Design Alternate Op Amps

	OPA322	OPA350
V_{SS}	1.8V to 5.5V	2.7V to 5.5V
V_{inCM}	Rail-to-rail	Rail-to-rail
V_{out}	Rail-to-rail	Rail-to-rail
V_{os}	2mV	0.15mV
I_q	1.9mA	5.2mA
I_b	10pA	0.5pA
UGBW	20MHz	38MHz
SR	10V/ μ s	22V/ μ s
#Channels	1, 2, 4	1, 2, 4
	www.ti.com/product/OPA322	www.ti.com/product/OPA350

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](#) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2022, Texas Instruments Incorporated