# **Reduce buck-converter EMI and voltage stress by minimizing inductive parasitics**

#### **By Timothy Hegarty**

Systems Engineer, Non-Isolated Power Solutions

#### Introduction

High-frequency conducted and radiated emissions from synchronous buck converters occur based on the transient voltage (dv/dt) and transient current (di/dt) generated during hard switching. Such electromagnetic interference (EMI) is an increasingly vexing issue in the design and qualification cycle, especially given the increased switching speed of power MOSFETs. This article identifies the significant role of power-stage inductive parasitics in EMI generation and offers suggestions for their minimization to reduce the broadband EMI signature.

## Critical converter loops with high slew-rate currents

A compact, optimized layout of a power stage lowers EMI for easier regulatory compliance. In translating a converter schematic to a board layout, one essential step is to pinpoint the high slew-rate current loops, with an eye to recognizing the layout-induced parasitic or stray inductances that cause excessive noise, overshoot, ringing and ground bounce.<sup>[1]</sup>

Consider the turn-on of the high-side MOSFET,  $Q_1$ , in the synchronous buck converter of Figure 1. Current flowing originally from source to drain of the synchronous MOSFET,  $Q_2$ , ramps to zero, and the current in  $Q_1$ increases to the inductor current level. Hence, the loop shaded in red and labeled "1" in Figure 1 is designated as the high-frequency switching power loop (or "hot" loop).

In contrast, the current flowing in the inductor,  $L_F$ , is largely DC with superimposed triangular ripple. The rate of change of the current is inherently limited by the inductor and any parasitic inductance contributed by the series connections is essentially benign.

Loops 2 and 3 in Figure 1 are classified as gate loops for the power MOSFETs. Specifically, loop 2 represents the high-side MOSFET's gate driver supplied by bootstrap capacitor,  $C_{BOOT}$ . Likewise, loop 3 corresponds to the low-side MOSFET's gate driver supplied by  $V_{CC}$ . The gate turn-on and turn-off current paths are delineated in each case by solid and dashed lines, respectively.



#### **Parasitic inductances**

In general, the behavior of MOSFET switching and the consequences for waveform ringing, power dissipation, device stress, and EMI are correlated with the parasitic inductances of the power-loop and gate-drive circuits. Figure 2 provides a comprehensive illustration of the parasitic elements arising from component placement, device package, and printed circuit board (PCB) layout routing that affect switching performance and EMI of the synchronous buck converter.

The effective high-frequency power-loop inductance,  $L_{LOOP}$ , is the sum of the total drain inductance,  $L_D$ , and the common-source inductance,  $L_S$ , that results from the series inductance of the input capacitor and PCB traces, and the package inductances of the power MOSFETs. As

expected, the power-loop inductance is highly related to the layout geometry of the input capacitor-MOSFET loop denoted by the red-shaded area in Figure 1.

Meanwhile, the gate-loop self-inductance,  $L_G$ , includes lumped contributions from the MOSFET package and PCB trace routing. An inspection of Figure 2 reveals that the common-source inductance of  $Q_1$  exists mutually in both the power and gate loops. It increases switching loss because the di/dt of the power loop creates a negative feedback voltage that impedes rise and fall times of the gate-source voltage. Another factor that leads to increased component stress is the common-source inductance of  $Q_2$ , which contributes to spurious turn-on of the low-side MOSFET during body-diode reverse recovery.<sup>[2]</sup>





#### **EMI frequencies and coupling modes**

Delineated in Table 1 are the three loosely-defined frequency ranges over which a synchronous buck converter excites and propagates EMI. During MOSFET switching, where the slew rate of the commutating current may exceed 5 A/ns, just 2 nH of parasitic inductance results in a voltage overshoot of 10 V. Furthermore, the current waveforms in the power loop with fast switching edges and leading-edge resonant ringing are rich in harmonic content, posing a severe threat of magnetic field coupling and radiated EMI.

Converter Domina Noise Type Sou		Dominant Noise Source	Frequency Range	Conducted/ Radiated Emissions
1	Low- frequency noise	Switching-frequency harmonics	150 kHz to 50 MHz	Conducted
2	Broadband noise	MOSFET voltage and current rise/ fall times, resonant ringing	50 MHz to 200 MHz	Both
3	High- frequency noise	Body-diode reverse recovery	Above 200 MHz	Radiated

#### Table 1. Converter EMI frequency classification

To get an idea of the harmonic frequency amplitudes of the switch (SW) voltage waveform, consider an input having a periodic trapezoidal pulse with finite rise and fall times (Figure 3). Using Fourier analysis, it is shown that the harmonic-amplitude envelope is a double-sinc function with corner frequencies of  $f_1$  and  $f_2$ , depending on the pulse width and rise/fall time of the time-domain waveform.<sup>[3]</sup> A similar analysis applies for the instantaneous current in the power loop.

- Three dominant noise-coupling paths are identified as:
- (1) conducted noise through the DC input lines;
- (2) magnetic field coupling from the power loop; and
- (3) electric field coupling from the SW-node copper surface.<sup>[4]</sup>

Power-loop inductance,  $L_{LOOP}$ , increases MOSFET switching loss and the peak drain-to-source voltage spike. It also exacerbates SW-voltage ringing, affecting broadband EMI in the 50- to 200-MHz range. Clearly, it is vital to minimize the effective loop length and enclosed area of the power loop. This reduces parasitic inductance and magnetic field self-cancellation, and makes it possible to reduce the magnetically-coupled radiated energy emanating from what effectively is a loop antenna structure.<sup>[3, 4, 5]</sup>

Conducted noise coupling is most likely on the converter input side as the ratio of loop inductance and input-capacitor series inductance (ESL) determines the filtering. Reducing  $L_{LOOP}$  increases the input-filter attenuation requirement. Fortunately, the noise conducted to the output is minimal if the filter inductor has a high self-resonant frequency (SRF) and also provides high transfer impedance from the SW to  $V_{OUT}$  nets. The output noise is additionally filtered by low-impedance output capacitor(s).



Texas Instruments

#### Equivalent resonant circuit

Referring to the SW voltage waveform in Figure 4, a resonance is excited by the parasitic energy stored during MOSFET switching. Simplified equivalent circuits are included on the right side of Figure 4 for analyzing the switching behavior. The switch-voltage overshoot above  $V_{\rm IN}$  and undershoot below ground (GND) are evident during the rising and falling edges, respectively. The oscillation amplitude depends on the distribution of partial inductances within the loop, and the subsequent ringing is damped by the effective loop AC resistance. This

contributes to voltage stress of the MOSFETs and gate drivers, and it also correlates to the frequency at which the broadband-radiated EMI is centered.<sup>[4]</sup>

Note that two important aspects during resonance are the resonant frequency and the loss or damping factor at that resonance. The main design goal is to push the resonant frequency as high as possible by minimizing the power-loop inductance. This decreases the stored reactive energy and lowers the resonant peak voltage. Also, the damping factor is increased at a higher frequency due to the skin effect.



#### EMI mitigation begins at the schematic

When studying a converter schematic prior to PCB layout, it is often convenient to highlight the high-current traces, the high-dv/dt circuit nodes, and the noise-sensitive nets, as shown in Figure 5. This example shows a 2.2-MHz converter intended for noise-sensitive automotive applications that uses a current-mode synchronous-buck controller, such as TI's LM5141-Q1.

#### **EMI** mitigation at the PCB

Minimizing the physical size of the loop by paying attention to component placement is central to reducing powerloop impedance. Noise coupling also depends on field distribution and orientation, making design of the PCB's inner layers also important.

A passive shield layer (Figure 6) is established using a ground plane as close as possible to the switching loop by

using minimum dielectric thickness. The horizontal current flow on the top layer sets up a vertical flux pattern. The resultant magnetic field induces a current in the shield layer opposite in direction to the current in the switching loop. By Lenz's law, the current in the shield layer generates a magnetic field to counteract the originating magnetic field. The result is H-field self-cancellation that results in lower parasitic inductance relative to what the loop area would suggest.<sup>[4]</sup>

Having an uninterrupted, continuous shield plane on layer 2 with close proximity to the switching loop offers optimal performance for enhanced suppression of RF energy, and its importance cannot be overstated. Low intra-layer z-axis spacing is specified in the PCB stack-up specification, for example by using a 5-mil core dielectric.<sup>[6]</sup> Shield-layer effectiveness is maximized by avoiding vias to the extent that all of the noise current is kept on the top layer.



Figure 6. Single-sided power stage component placement (top view)



Provisioning for EMI also places an emphasis on a small SW-node copper area to reduce capacitive coupling related to high-dv/dt SW-node voltage swings. The SW-node copper pour should be short and wide. A full ground plane under the SW node contributes a very small increase in SW-to-GND parasitic capacitance, but is recommended for a multi-layer stack-up PCB to diminish the electrically-coupled radiated energy.<sup>[5]</sup> A copper-pour keepout is maintained on the top layer under the inductor to minimize capacitive coupling from SW to V<sub>OUT</sub>.

#### **EMI** mitigation using controller features

When the PCB layout is fixed, various noise-reduction features integrated in synchronous buck controllers are most useful when dealing with EMI in the latter design stages. For example, the LM5141-Q1 includes asymmetric gate-drive slew-rate control, external clock synchronization, an internal oscillator, and on-the-fly frequency hopping for adaptive tuning to avoid sensitive AM radio bands in automotive systems. Pulse skipping at light loads is inhibited during synchronization, or when the DEMB/ SYNC pin is pulled low to reduce noise and RF interference. For added reliability, this device is rated for negative SW-node and gate-drive transients of -5 V with up to 20-ns duration.

To further diminish the EMI signature, a novel technique of spread-spectrum frequency modulation (SSFM), also known as dithering, disperses the spectral energy of the switching signal. Based on the CISPR 25 class 5 automotive specification, Figure 7 shows a substantial improvement in conducted emissions when spread-spectrum is enabled with the LM5141-Q1.

#### Conclusion

Synchronous buck converters generally switch under 3 MHz, but generate broadband noise and EMI up to 1 GHz. Understanding the key converter switching loops from the schematic and diligently minimizing these loop areas during PCB design is imperative to reduce both conducted and radiated EMI. Controller-integrated EMI mitigation techniques, such as dither and slew-rate control, are convenient options in the latter design phases when a PCB spin is unacceptable.

#### References

- 1. Timothy Hegarty, "DC/DC converter PCB layout," Part 1, Part 2 and Part 3, EDN, June 2015
- 2. J. Wang and H. Shu-Hung, "Impact of Parasitic Elements on the Spurious Triggering Pulse in Synchronous Buck Converter," IEEE Trans. on Power Electronics, Dec. 2010, pp. 6672-6685
- 3. M. Montrose, "Printed Circuit Board Design Techniques for EMC Compliance: A Handbook for Designers," 2nd Ed., IEEE press, 2000

#### Figure 7. CISPR 25 class 5 conducted emissions measurement from 150 kHz to 30 MHz



- 4. Ankit Bhargava, David Pommerenke, Keong W. Kam, Federico Centola and Cheng Wei Lam, "DC-DC Buck Converter EMI Reduction Using PCB Layout Modification," IEEE Trans. on EMC, August 2011, pp. 806–813
- 5. "Layout Tips for EMI Reduction in DC/DC Converters," TI Application Report (SNVA638A), April 2013
- "Layout Considerations for LMG5200 GaN Power Stage," TI Application Report (SNVA729A), September 2015

#### **Related Web Sites**

Product information: LM5141-Q1 LM5140-Q1

Visit www.ti.com/aaj to see all AAJ articles.

## TI Worldwide Technical Support

### **Internet**

**TI Semiconductor Product Information Center Home Page** support.ti.com

#### TI E2E<sup>™</sup> Community Home Page

e2e.ti.com

## **Product Information Centers**

Americas	Phone	+1(512) 434-1560
Brazil	Phone	0800-891-2616
Mexico	Phone	0800-670-7544
Interr	Fax net/Email	+1(972) 927-6377 support.ti.com/sc/pic/americas.htm

#### Europe, Middle East, and Africa

Phone

European Free Call	00800-ASK-TEXAS (00800 275 83927)
International	+49 (0) 8161 80 2121
Russian Support	+7 (4) 95 98 10 701

**Note:** The European Free Call (Toll Free) number is not active in all countries. If you have technical difficulty calling the free call number, please use the international number above.

Fax	+(49) (0) 8161 80 2045
Internet	www.ti.com/asktexas
Direct Email	asktexas@ti.com

#### Japan

Fax	International	+81-3-3344-5317
	Domestic	0120-81-0036
Internet/Email	International	support.ti.com/sc/pic/japan.htm
	Domestic	www.tij.co.jp/pic

E2E is a trademark of Texas Instruments. All other trademarks are the property of their respective owners.

#### Asia

Phone	Toll-Free Number			
Note: Toll- mobile and	<b>Note:</b> Toll-free numbers may not support mobile and IP phones.			
Australia	1-800-999-084			
China	800-820-8682			
Hong Kong	800-96-5941			
India	000-800-100-8888			
Indonesia	001-803-8861-1006			
Korea	080-551-2804			
Malaysia	1-800-80-3973			
New Zeala	nd 0800-446-934			
Philippines	1-800-765-7404			
Singapore	800-886-1028			
Taiwan	0800-006800			
Thailand	001-800-886-0010			
International	+86-21-23073444			
Fax	+86-21-23073686			
Email	tiasia@ti.com or ti-china@ti.com			
Internet	support.ti.com/sc/pic/asia.htm			

Important Notice: The products and services of Texas Instruments Incorporated and its subsidiaries described herein are sold subject to TI's standard terms and conditions of sale. Customers are advised to obtain the most current and complete information about TI products and services before placing orders. TI assumes no liability for applications assistance, customer's applications or product designs, software performance, or infringement of patents. The publication of information regarding any other company's products or services does not constitute TI's approval, warranty or endorsement thereof.

A021014

 $\ensuremath{\textcircled{}}$  2016 Texas Instruments Incorporated. All rights reserved.



SLYT682

#### **IMPORTANT NOTICE**

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have *not* been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products		Applications	
Audio	www.ti.com/audio	Automotive and Transportation	www.ti.com/automotive
Amplifiers	amplifier.ti.com	Communications and Telecom	www.ti.com/communications
Data Converters	dataconverter.ti.com	Computers and Peripherals	www.ti.com/computers
DLP® Products	www.dlp.com	Consumer Electronics	www.ti.com/consumer-apps
DSP	dsp.ti.com	Energy and Lighting	www.ti.com/energy
Clocks and Timers	www.ti.com/clocks	Industrial	www.ti.com/industrial
Interface	interface.ti.com	Medical	www.ti.com/medical
Logic	logic.ti.com	Security	www.ti.com/security
Power Mgmt	power.ti.com	Space, Avionics and Defense	www.ti.com/space-avionics-defense
Microcontrollers	microcontroller.ti.com	Video and Imaging	www.ti.com/video
RFID	www.ti-rfid.com		
OMAP Applications Processors	www.ti.com/omap	TI E2E Community	e2e.ti.com
Wireless Connectivity	www.ti.com/wirelessconn	ectivity	

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265 Copyright © 2016, Texas Instruments Incorporated