

Multichannel Analog Input Modules for PLC Equipment

Tamara Alani, Tim Green, Ahmed Noeman



Introduction

A Programmable Logic Controller (PLC) is a ruggedized computer modified system specifically for manufacturing process control, such as automated assembly lines, robotic machines, and other high reliability control which requires flexible programming and fault diagnostics.

PLCs are often comprised of many different types of input modules to monitor real world parameters or receive analog or digital input command signals from other PLCs, central control computers, or human interface devices.

The Analog Input Module (AIN) is a key subsystem in the PLC. AINs come in many variations to condition real world physical parameters, such as, Temperature, Pressure, Force, or Strain. Typically, these AIN inputs are command signals in both voltage (e.g. $\pm 10V$) and current form (e.g. 4-20mA).

A Multi-Channel AIN is often preferred for its flexibility, space-efficiency and power- efficiency when compared to many single channel, dedicated input modules. As seen in Figure 1 below, multiple channels share processing, analog inputs, backplane power and communication.

Different Multi-Channel, AIN architectures will be compared for optimum system configuration.

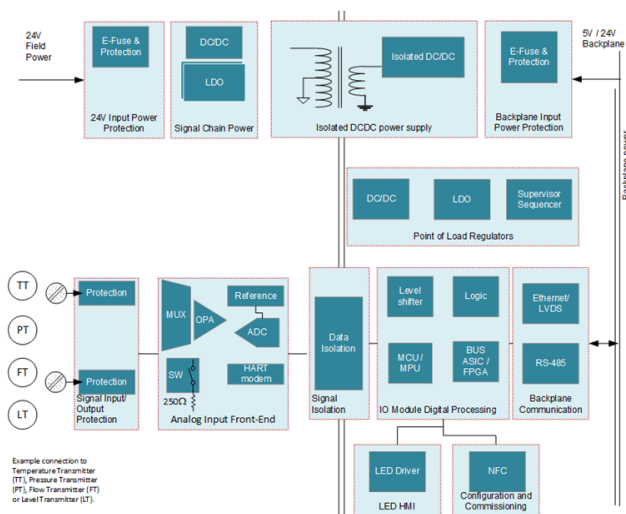


Figure 1. Reference Diagram for Multi-Channel AIN

AIN Architecture Overview

Four different, typical architectures for a multi-channel AIN are to be reviewed: Channel-to-Channel Isolated, Simultaneous Sampling, Multiplexed Inputs with Integrated MUX, and Multiplexed Inputs with External MUX. For more detailed information on these systems, visit the TI website for [Analog Input Modules](#).

Channel-to-Channel Isolated

For high-voltage isolation (usually in the kV range), channel-to-channel isolated modules are used. See Figure 2 for an overview of this architecture. This approach yields very high common mode rejection (CMR), and high voltage isolation since the channels do not share ground. Generally in Channel-to-Channel Isolated modules, each channel uses a separate AFE (Analog Front End), ADC (Analog-to-Digital Converter), data isolator and isolated power.

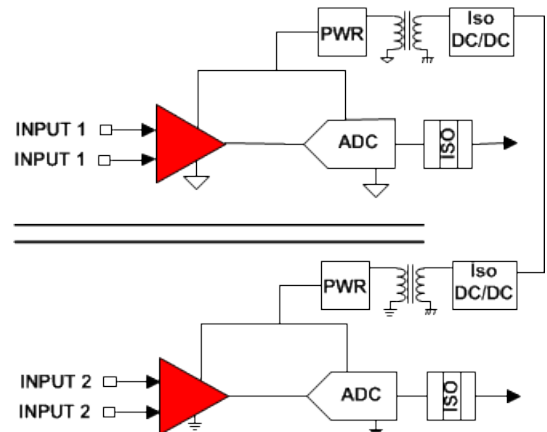


Figure 2. Channel-to-Channel Isolated

Simultaneous Sampling

For very high bandwidth systems, or if accurate measurement of the phase relation between channels is required, simultaneous sampling is used. A typical end application for this would be motor control or power monitoring. The Simultaneous Sampling architecture, shown in Figure 3 below, is used to achieve accurate signal when minimal phase shift between the inputs is essential. The [ADS8578S](#) is a 14-Bit, High Speed, 8-Channel, Simultaneous-Sampling ADC with Bipolar Inputs from a Single Supply. In addition it has an integrated reference and reference buffer.

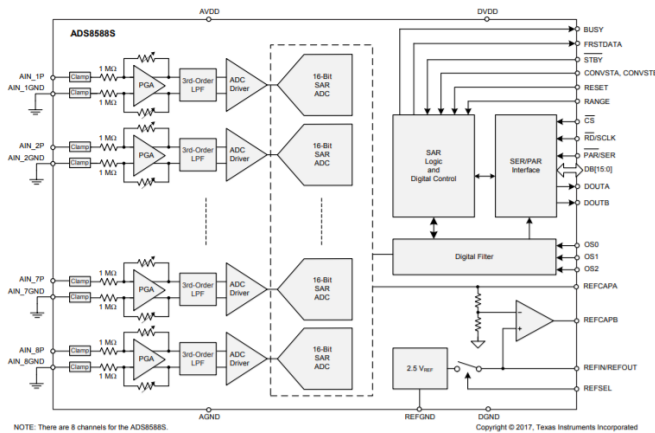


Figure 3. Simultaneous Sampling

Multiplexed Inputs with Integrated MUX

The remaining two Multi-Channel AIN modules use multiplexed-inputs. An integrated MUX and ADC solution is shown below in Figure 4. This type of solution is suitable for lower power and smaller footprint requirements. With any level of integration comes performance trade-offs based on process constraints to get the best of the analog and the best of the mixed signal.

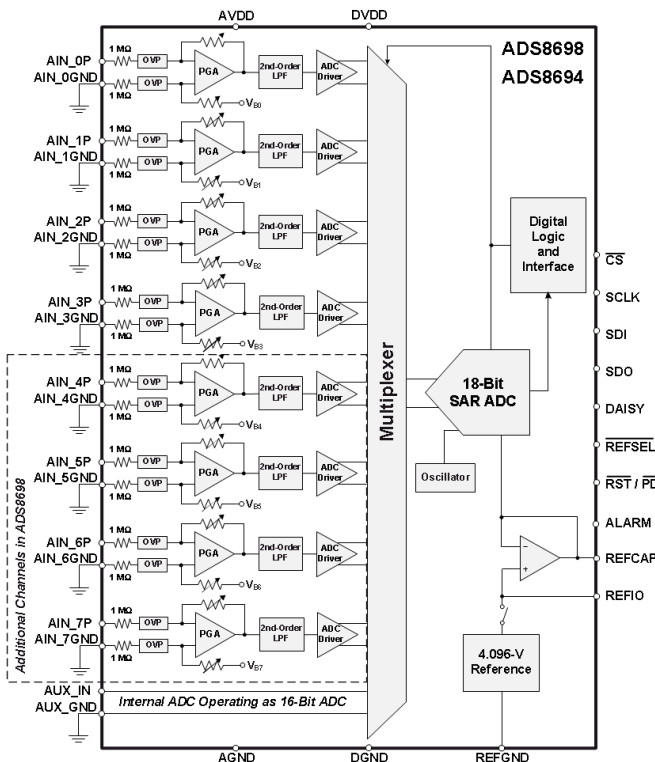


Figure 4. Multiplexed Inputs with Integrated MUX

Multiplexed Inputs with External MUX

One of the most common approaches when designing for maximum flexibility of performance and cost uses discrete Op Amps, an ADC and MUX as shown in Figure 5 below. This is a common approach when flexibility for performance and cost is preferred. Each analog input signal scaling can be custom tailored for a specific type and range of signal as well as desired noise and frequency filtering. This signal chain uses a drive op amp circuit after the MUX into the ADC, and possibly an ADC reference buffer. A **MUX-Friendly** amplifier such as the **OPAx189** or **OPAx192** can be used after the MUX, such as **MUX36S08** or **MUX36D04**, to switch between channels to accomplish fast settling time. If a reference buffer is needed, see TI's 20MHz, high-precision **OPA320**.

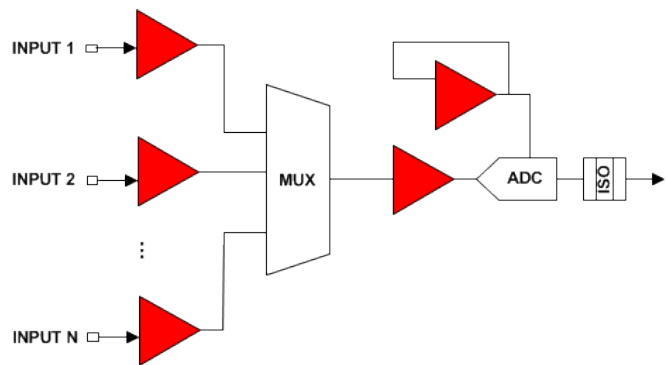


Figure 5. Multiplexed Inputs with External MUX

Table 1. Referenced Devices

Device	Feature
OPA189	MUX-Friendly, Zero-Drift , 36V, 14MHz, 3μV offset, 5.2nV/√Hz noise
OPA192	MUX-Friendly, E-Trim , 36V, 10MHz, 25μV offset, 5.5nV/√Hz noise
OPA388	MUX-Friendly, Zero-Drift, Zero-Crossover , 5V, 10MHz, 5μV offset, 7nV/√Hz noise
OPA320	Zero-Crossover , 5V, 20MHz, 0.9pA bias current, 150μV offset, 8.5nV/√Hz noise
ADS5888S	16-Bit High-Speed 8-Channel Simultaneous-Sampling ADC
MUX36S08	36-V, Low-Capacitance, Low-Leakage-Current, Precision, Analog Multiplexers
MUX36D04	

Table 2. Related Documentation

Literature number:	Description
SBOT040	MUX-Friendly Precision Op Amps
SBOA182B	Zero-Drift Amps: Features and Benefits
SBOA181A	Zero-Crossover Amps: Features and Benefits
SBOT037A	Offset Correction: Laser Trim, e-Trim, and Chopper

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (www.ti.com/legal/termsofsale.html) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2019, Texas Instruments Incorporated