## Benefits of a Low Inductive Shunt for Current Sensing in PWM Applications

### Arjun Prakash, Current Sensing Products

# Texas Instruments

Current sensing in a Pulse Width Modulation (PWM) systems presents challenge due to large change in common mode voltage(s). In PWM systems, for in-line current sensing the current sense amplifier should have the ability to reject high dv/dt common mode signals and accurately measure the voltage drop across the shunt which will produce the di/dt information of the load, which is predominantly inductive.

INA240 current sense amplifier was specifically designed to work in PWM applications that can reject the high dv/dt signals and accurately measure the di/dt information. The fast PWM rejection feature assists in fast settling of dv/dt signals so the amplifier can accurately track the di/dt information. INA240 can provide very accurate fast real time current in a PWM switching signal. The key to achieving accuracy in PWM system is a combination of INA240 and a very precise high accuracy, low ohmic, low temperature drift and low inductive shunt. The INA240 amplifies the signal across the shunt and produces the output. As PWM switching signals have sharp edges a series parasitic capacitance or inductance introduced by the shunt is directly seen at the input of the INA240 which is hence amplified at the output. This is one of the common examples of reduced current accuracy.

One of the key system requirements for accurate current sensing in a PWM application is the low inductive shunt. Shunt resistors are comprised of metal, ceramic compound and carbon materials. The ceramic and carbon components add additional parasitic inductance to the effective shunt of the amplifier. Shunt manufacturers do produce lowinductive shunts, these should be chosen for accurate PWM current measurements. For DC current measurements the parasitics of the inductance can be ignored because at DC the inductance acts as a short and it behaves as a parasitic resistor. The effective parasitic resistance of the inductor is insignificant compared to the value of the shunt. Typically if the PWM signals are <1Khz the parasitic inductance of the shunt can be ignored.



#### Figure 1. Effective Impedance of a Shunt Resistor

Figure 1 illustrates the effective impedance of shunt resistor. For DC measurements the voltage across the shunt resistor is  $V = I \times R$ . For AC and PWM currents the voltage developed across the shunt resistor will be  $V = I \times R + L \times di$ ; dt. As the inductance of the shunt increases the error voltage developed across the shunt increases and as the PWM frequencies increase the voltage error further increases. For accurate PWM current measurements a system with a shunt resistor with low inductance is required. When identifying a shunt, the data sheet will have a specification of inductance. A typical low inductive shunt from shunt manufacturers ranges from 3nH to 5nH. Shunt manufacturers use low inductive ceramic and carbon materials to achieve such low inductance. Few manufacturers do produce shunt using special metal alloys with low temperature drift which are trimmed. These shunts are bulky and often used for applications that require 500A of current or higher.

#### Current Sensing in a DC-DC Converter

Figure 2 illustrates an example of in-line current sensing for a DC-DC converter. The PWM switching frequencies can be in the order of 100Khz to 1Mhz. At such high frequencies the parasitics related to board layout and type of shunt selected plays a crucial role in achieve high accuracy. Any additional large inductance in series with the PWM node shunt introduces glitches and overshoot. These glitches and the overshoot which will be at the input of the current sense amplifier. A current sense amplifier with a gain will amplify the overshoot and corrupting the signal

1



www.ti.com

integrity. One technique to minimize input glitches to the current sense amplifier is to add additional input filter but such implementation reduces the bandwidth and hence lowers the response time for critical alert techniques.



Figure 2. Current Sensing in a DC-DC Converter

Figure 3 describes the wavefroms in a DC-DC converter system. The waveform includes the PWM input to the shunt and the various voltage errors developed across the shunt with parasitic inductance. Ideally if the shunt has no parasitic inductance the voltage developed across the shunt will be proportional to output load current. Since the shunt has a finite parasitic inductance the total error developed across the shunt will be a summation of load current and the current developed across the parasitic inductance (Le). The error in the current measurement can be minimized by lowering the inductance in the shunt.



Figure 3. Output Waveforms in DC-DC Converter

2

#### Low inductive Shunt in Motor Control

In a motor control application, as the motor windings age due to continuous usage the efficiency of the motor drops. This is usually an indication of early failure of the motor. One of the benefits of low inductive current shunt is a motor control is to identify and detect winding to winding shorts. The effective inductance in the motor is made up of copper wire wound over several times across the core. If a short exists between the windings, detecting a change in inductance of the motor can help identify motor failures and can prevent costly system downtime and permanent motor damage. A low inductive shunt in series with the PWM can benefit in detecting minor changes in inductance.

INA240 is a high precision, bi-directional current sense amplifier with low input offset and gain drift across temperature range making it an ideal device for measuring currents in a PWM application. The INA240 is specifically designed to work in switched node environments where the common mode transients will have large dv/dt signals. The ability to reject high dv/dt signals enables accurate current measurements. The true performance benefits of the current sensing can be achieved in combination with a low inductive shunt. The INA240 has low maximum input offset voltage of  $25\mu$ V and a maximum gain error of 0.2% allowing for smaller shunt resistance values to be used without sacrificing measurement accuracy. The offset drift and gain error drift is as low as 0.25µV/°C and 2.5ppm/°C respectively enabling accurate and stable current measurements across temperature.

#### Table 1. Alternate Device Recommendations

Device	Optimized Parameter	Performance Trade- Off
INA168	Bandwidth : 800kHz, Package: SOT-23	Adjustable gain, external components
LMP8601	$V_{CM}$ -22V to 60V	Offset voltage: 1mV, bandwidth: 60kHz
INA282	DC CMRR: 140dB	Bandwidth: 10kHz

#### Table 2. Related TI TechNotes

SBOA174	Current Sensing in an H-Bridge	
SBOA176	Switching Power Supply Current Measurements	
SBOA166	High-Side Drive, High-Side Solenoid Monitor With PWM Rejection	
SBOA162	Measuring Current To Detect Out-of-Range Conditions	

#### IMPORTANT NOTICE FOR TI DESIGN INFORMATION AND RESOURCES

Texas Instruments Incorporated ('TI") technical, application or other design advice, services or information, including, but not limited to, reference designs and materials relating to evaluation modules, (collectively, "TI Resources") are intended to assist designers who are developing applications that incorporate TI products; by downloading, accessing or using any particular TI Resource in any way, you (individually or, if you are acting on behalf of a company, your company) agree to use it solely for this purpose and subject to the terms of this Notice.

TI's provision of TI Resources does not expand or otherwise alter TI's applicable published warranties or warranty disclaimers for TI products, and no additional obligations or liabilities arise from TI providing such TI Resources. TI reserves the right to make corrections, enhancements, improvements and other changes to its TI Resources.

You understand and agree that you remain responsible for using your independent analysis, evaluation and judgment in designing your applications and that you have full and exclusive responsibility to assure the safety of your applications and compliance of your applications (and of all TI products used in or for your applications) with all applicable regulations, laws and other applicable requirements. You represent that, with respect to your applications, you have all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. You agree that prior to using or distributing any applications. TI has not conducted any testing other than that specifically described in the published documentation for a particular TI Resource.

You are authorized to use, copy and modify any individual TI Resource only in connection with the development of applications that include the TI product(s) identified in such TI Resource. NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information regarding or referencing third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of TI Resources may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI RESOURCES ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING TI RESOURCES OR USE THEREOF, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY YOU AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS EVEN IF DESCRIBED IN TI RESOURCES OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF TI RESOURCES OR USE THEREOF, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

You agree to fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of your noncompliance with the terms and provisions of this Notice.

This Notice applies to TI Resources. Additional terms apply to the use and purchase of certain types of materials, TI products and services. These include; without limitation, TI's standard terms for semiconductor products <a href="http://www.ti.com/sc/docs/stdterms.htm">http://www.ti.com/sc/docs/stdterms.htm</a>), evaluation modules, and samples (<a href="http://www.ti.com/sc/docs/stdterms.htm">http://www.ti.com/sc/docs/stdterms.htm</a>), evaluation

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265 Copyright © 2017, Texas Instruments Incorporated